Lecture 9, Feb 2, 2022

Simplifying Series and Parallel Resistors

• Two components are connected *in series* if they're connected back-to-back, and at the point of connection there is no other current path:

$$\sim \stackrel{R_1}{\longrightarrow} \stackrel{R_2}{\longrightarrow} \sim$$

• To find equivalent resistance in a series circuit, compare:

$$\begin{array}{c} + & + \\ & v_1 \swarrow R_1 & + \\ v_{tot} & - \\ & + \\ & v_{tot} & v_{eq} \swarrow R_{eq} \\ & + \\ & v_2 \swarrow R_2 \\ - & - \\ & & - \\ & & & & \\ \end{array}$$

- KVL gives: $-v_{tot} + v_1 + v_2 = 0$
 - * Applying Ohm's law: $v_1 = R_1 i_{tot}$ and $v_2 = R_2 i_{tot}$
 - * Substituting the voltages back in: $-v_{tot} + R_1 i_{tot} + R_2 i_{tot} = 0 \implies v_{tot} = (R_1 + R_2) i_{tot}$
 - * Compare this to Ohm's law for the second circuit, we see that the equivalent resistance is $R_1 + R_2$
 - * This generalizes to any number of resistors to give $R_{eq} = R_1 + R_2 + \cdots + R_n$
 - * In the extreme cases, if one resistor is an open circuit $R = \infty$, the entire circuit can be considered as an open connection; if one resistor is a short circuit, then it wouldn't have any effect
- Two components are connected *in parallel* if they share two common nodes:

• To find equivalent resistance in a parallel circuit, compare:

$$\begin{array}{c} \stackrel{}{\overset{}_{+}} & i_1 \\ \stackrel{}{\overset{}_{v_{tot}}} \\ \stackrel{}{\overset{}_{-}} \end{array} \xrightarrow{R_1} \begin{array}{c} \stackrel{}{\overset{}_{2}} \\ R_2 \\ \stackrel{}{\overset{}_{v_{tot}}} \\ \stackrel{}{\overset{}_{-}} \end{array} \xrightarrow{R_{eq}} \begin{array}{c} \\ R_{eq} \\ \stackrel{}{\overset{}_{-}} \end{array} \xrightarrow{R_{eq}} \begin{array}{c} \\ \\ \\ \end{array} \xrightarrow{R_{eq}} \end{array}$$

- KCL gives: $i_{tot} = i_1 + i_2$

* KVL gives: $v_{tot} = R_i i_1 = R_2 i_2 \implies i_1 = \frac{v_{tot}}{R_1}, i_2 = \frac{v_{tot}}{R_2}$

$$i_{tot} = \frac{1}{R_1} + \frac{1}{R_2}$$

* Compare this to circuit 2 we get $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \implies R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2}$

• Alternatively, the equivalent conductance of two resistors in parallel is the sum of the conductances

* The conductance relation generalizes to any number of resistors; however $\frac{R_1R_2}{R_1+R_2}$ becomes

 $\frac{R_1R_2R_3}{R_1R_2 + R_2R_3 + R_1R_3} \text{ for 3 resistors, } \frac{R_1R_2R_3R_4}{R_1R_2R_3 + R_1R_2R_4 + R_1R_3R_4 + R_2R_3R_4} \text{ and so on}$ * In the extreme cases, if one resistor is a short circuit, then the entire circuit can be considered

a short circuit; if one resistor is an open connection, then it does not have an impact (since $\frac{1}{R} \to 0$)